

Logic Design

Arash Sal Moslehian

2's Complement Two Bit Multiplier

We will refer to the first two bits as number A and the second two bits as number B.

Functions s, h, f, g will refer to the sign, the third bit, the second bit and the first bit respectively.

We have the following truth table for the 15 different inputs:

$A_1A_2B_1B_2$	$A \times B$	s	h	f	g
00 00	0×0	0	0	0	0
00 01	0×1	0	0	0	0
00 10	0×-2	0	0	0	0
00 11	0×-1	0	0	0	0
01 00	1×0	0	0	0	0
01 01	1×1	0	0	0	1
01 10	1×-2	1	0	1	0
01 11	1×-1	1	0	0	1
10 00	-2×0	0	0	0	0
10 01	-2×1	1	0	1	0
10 10	-2×-2	0	1	0	0
10 11	-2×-1	0	0	1	0
11 00	-1×0	0	0	0	0
11 01	-1×1	1	0	0	1
11 10	-1×-2	0	0	1	0
11 11	-1×-1	0	0	0	1

Now, all we have to do is simplify the functions using Karnaugh's Map.

$$s(A_1A_2B_1B_2) = \sum m(6, 7, 9, 13) = A_1\bar{B}_1B_2 + \bar{A}_1A_2B_1$$

$$h(A_1A_2B_1B_2) = \sum m(10) = A_1\bar{A}_2B_1\bar{B}_2$$

$$f(A_1A_2B_1B_2) = \sum m(6, 9, 11, 14) = A_2B_1\bar{B}_2 + A_1\bar{A}_2B_2$$

$$g(A_1A_2B_1B_2) = \sum m(5, 7, 13, 15) = A_2B_2$$

Function s

$B_1B_2 \backslash A_1A_2$	00	01	11	10
00				
01			1	1
11		1		
10		1		

Function f

$B_1B_2 \backslash A_1A_2$	00	01	11	10
00				
01				1
11				1
10		1	1	

Function g

$B_1B_2 \backslash A_1A_2$	00	01	11	10
00				
01		1	1	
11		1	1	
10				